

Versatile LED Driver Can Be Used with Input Voltages Above or Below the Level of the LED String

Victor Khasiev, Senior Applications Engineer

Introduction

The LTM8042 is a μ Module® LED driver capable of supporting LEDs with up to 1 A current and a 3000:1 dimming ratio. It operates from input voltages of 3 V to 30 V and a wide frequency range of 250 kHz to 2 MHz, enabling its use in a wide array of applications, such as scanners and automotive and avionic lighting.

The LTM8042 can be easily configured in three topologies—boost, buck, and buck-boost—to meet a wide variety of specific application requirements. For low input voltages and high string voltages, a boost topology is appropriate, whereas a buck is more suitable for high input voltages and low string voltages. A buck-boost topology is used for a wide range of inputs where voltage can be below or above the LED string. This article covers the process of selecting the suitable topology and its corresponding connections.

Boost LED Driver

The most common topology for an LED driver is a boost application, as might be used for an LED array powered from a 12 V input rail, where $V_{\text{IN}} < V_{\text{F}}.$ An LTM8042 boost solution is shown in Figure 1 with a block diagram shown in Figure 2. The input voltage is connected to the BSTIN/BKLED— terminal and the LED string cathode is connected to GND. When transistor Q is on, the current builds up in the inductor L. Once Q turns off, the voltage across L changes polarity and the inductor current begins flowing to output filter capacitor C2. LED dimming is implemented in the PWM section, which regulates the duty cycle, and by extension the average LED current (set by resistor RCLR). Capacitor C1 is an input voltage filter.

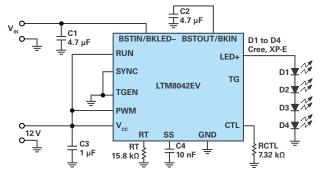


Figure 1. The LTM8042 driving four LEDs where $V_{IN} = 5.75 \text{ V}$ to 10.25 V and $I_{OUT} = 0.5 \text{ A}$.

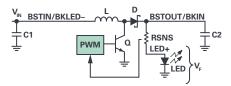


Figure 2. LTM8042 block diagram connections in boost configuration.

Buck LED Driver

A buck topology is used for relatively high input voltages, such as automotive and industrial 24 V rails. Figure 3 shows a block diagram for a configuration for $V_{\text{IN}} > V_{\text{F}}$. The input voltage connected to the BSTOUT/BKIN terminal and LED cathode connected to the BSTIN/BKLED— terminal. When transistor Q is on, current flows from the input through the LED string and inductor L to GND. Once Q turns off, the voltage across L changes polarity and diode D becomes forward biased, pulling the LED cathode below the input voltage level, providing the set value of the current in the LED string. C5 creates an output filter for this topology.

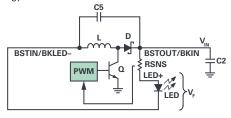


Figure 3. LTM8042 block diagram connections in buck configuration.

Buck-Boost LED Driver

In many commercial, battery, and solar-powered applications, the input voltage varies over a wide range. In these situations, the buck-boost topology shown in Figure 4 is best. The input voltage and LED cathode are connected to the BSTIN/BKLED— terminal. When transistor Q is on, the current builds in inductor L. Once Q turns off, the voltage across L changes polarity, forward biasing diode D while the voltage climbs above the input level. The PWM maintains the set value of current through the LED and C5, and the C2 functions as an output filter. The LED string voltage V_F can be below or above V_{IN} .

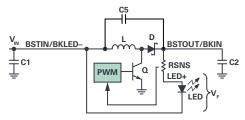


Figure 4. LTM8042 block diagram connections in buck-boost configuration.

Test Results for the Three Topologies

All three topologies were tested using the DC1511 demonstration circuit featuring the LTM8042—using the same LED string, output current, and switching frequency in all cases. To make sure that bias power dissipation is the same for all three settings, the same $V_{\rm CC}$ (shown in Figure 1) was supplied as well. The $V_{\rm CC}$ pin can be tied to $V_{\rm IN}$ in most cases. Figure 5 shows the resulting efficiency curves. All three topologies were also modeled in LTspice® environments and simulation files related to LTM8042 can be found in its data sheet.

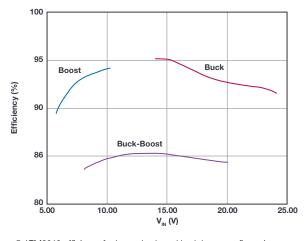


Figure 5. LTM8042 efficiency for boost, buck, and buck-boost configurations.

Conclusion

LTM8042 is a versatile and efficient LED driver capable of operating over a wide input voltage range, while providing up to 1 A LED string current. The LTM8042 is easily applied as a boost, buck, or buck-boost driver to satisfy the needs of a wide variety of applications.

About the Author

Victor Khasiev is a senior applications engineer at Analog Devices with extensive experience in power electronics both in ac-to-dc and dc-to-dc conversion. He holds two patents and has written multiple articles. These articles relate to the use of ADI semiconductors in automotive and industrial applications. They cover step-up, step-down, SEPIC, positive-to-negative, negative-to-negative, flyback, and forward converters, as well as bidirectional backup supplies. His patents concern efficient power factor correction solutions and advanced gate drivers. Victor enjoys supporting ADI customers by answering questions about ADI products, designing and verifying power supply schematics, laying out print circuit boards, trouble-shooting, and participating in testing final systems. He can be reached at *victor.khasiev@analog.com*.

Online Support Community



Engage with the

Analog Devices technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.

Visit ez.analog.com

